

Chapter 3 Inductance and Capacitance

1. Current –voltage relationship for a capacitance or inductance.
2. Stored energy in a capacitance or inductance.

Chapter 3
Inductance and Capacitance

Capacitors: Concept


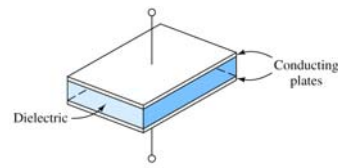


Figure 3.1 A parallel-plate capacitor consists of two conductive plates separated by a dielectric layer.

- A capacitor consists of two conducting plates
- Charge builds up on each of the plates
- Energy **storage** element via electrical field

Chapter 3
Inductance and Capacitance

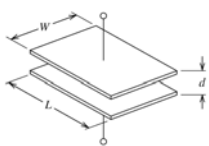Capacitance of the Parallel-Plate Capacitor



$$C = \frac{\epsilon A}{d} \quad A = WL$$

$$\epsilon_0 \cong 8.85 \times 10^{-12} \text{ F/m}$$

$$\epsilon = \epsilon_r \epsilon_0$$

Table 3.1: Dielectric constants
Example: Air – 1.0

Chapter 3
Inductance and Capacitance


Relationship: Voltage-current

$$q = Cv \quad C: \text{Capacitance in Farads}$$

$$i(t) = \frac{dq}{dt}$$

$$i = C \frac{dv}{dt}$$
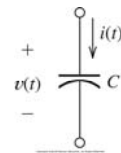
$$v(t) = \frac{1}{C} \int_{t_0}^t i(t) dt + v(t_0)$$



Passive Configuration

Chapter 3
Inductance and Capacitance

Example 3.1

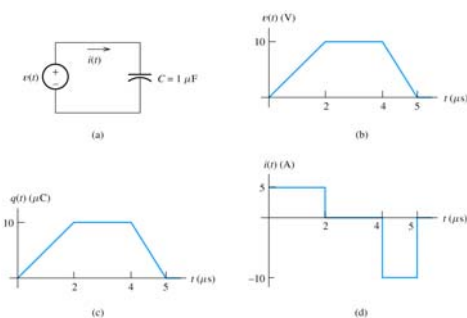


Figure 3.4 Circuit and waveforms for Example 3.1.

Chapter 3
Inductance and Capacitance

Example 3.2

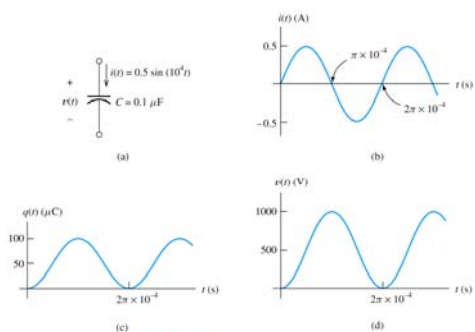


Figure 3.5 Waveforms for Example 3.2.

Chapter 3
Inductance and Capacitance

Power $p(t) = v(t)i(t)$ $p(t) = Cv(t)\frac{dv}{dt}$

Stored Energy $w(t) = \int_{t_0}^t p(t)dt$

$$w(t) = \int_{t_0}^t Cv(t)\frac{dv}{dt}dt$$

$$= \int_0^{v(t)} Cv(t)dv \quad v(0) = 0$$

$$= \frac{1}{2}Cv(t)^2$$

Chapter 3
Inductance and Capacitance

Example 3.3

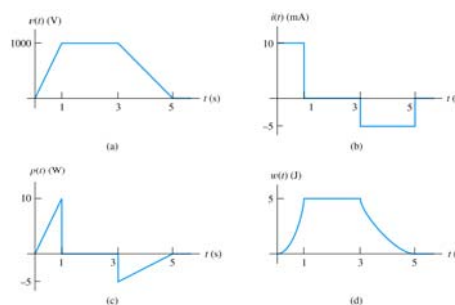


Figure 3.6 Waveforms for Example 3.3.

Chapter 3
Inductance and Capacitance

Exercise 3.2

Find out charge, voltage, power and energy

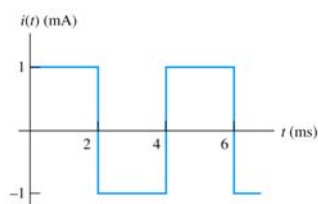


Figure 3.7 Square-wave current for Exercise 3.2.

Chapter 3
Inductance and Capacitance

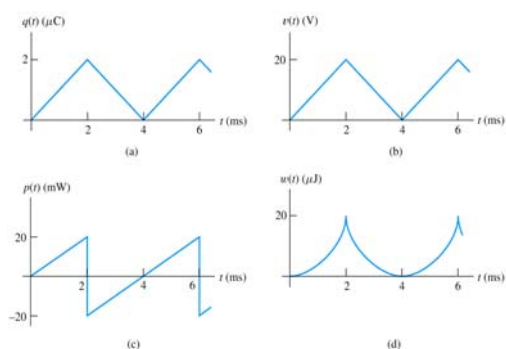


Figure 3.8 Answers for Exercise 3.2.

Chapter 3
Inductance and Capacitance

Questions

If a **DC** voltage is applied, what is the current?

Can the current change *instantly*?

Can the voltage change *instantly*?

How much energy does a capacitor dissipate?

Chapter 3
Inductance and Capacitance

Capacitance in parallel

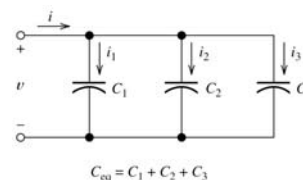


Figure 3.9 Three capacitances in parallel.

Chapter 3
Inductance and Capacitance

Capacitance in series

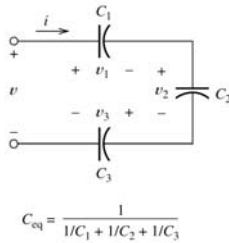


Figure 3.11 Three capacitances in series.

Chapter 3
Inductance and Capacitance

Real Model of practical capacitors

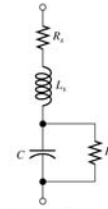


Figure 3.14 The circuit model for a capacitor including the parasitic elements R_s , L_s , and R_p .

Chapter 3
Inductance and Capacitance

Inductors


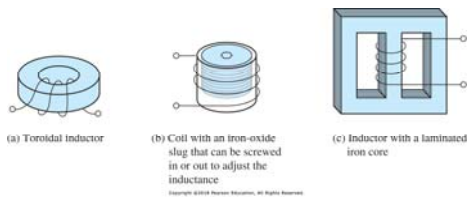


Figure 3.16 An inductor is constructed by coiling a wire around some type of form.

- An inductor is a coil of conducting wire wrapped around some magnetic material
- Energy **storage** element via magnetic field

Chapter 3
Inductance and Capacitance

Relationship: Voltage-current

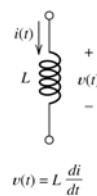

$$v(t) = L \frac{di}{dt}$$

$$i(t) = \frac{1}{L} \int_{t_0}^t v(t) dt + i(t_0)$$

$$w(t) = \frac{1}{2} Li^2(t)$$

Chapter 3
Inductance and Capacitance

Example 3.7

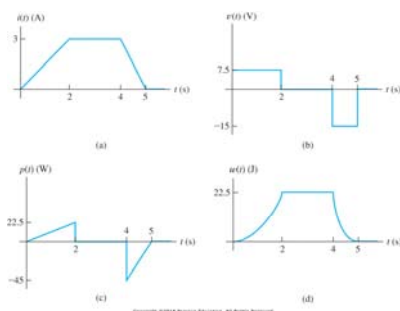


Figure 3.18 Waveforms for Example 3.7.

Chapter 3
Inductance and Capacitance

Example 3.8

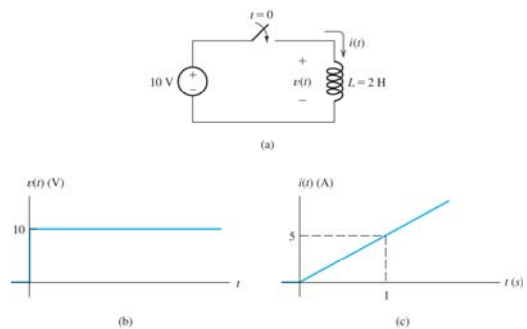


Figure 3.19 Circuit and waveforms for Example 3.8.

Chapter 3
Inductance and Capacitance

Exercise 3.7: Find current

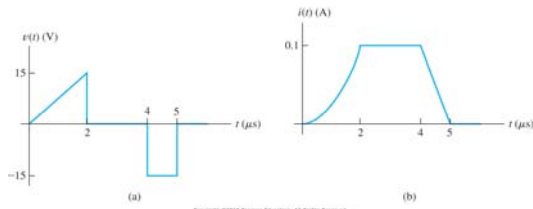


Figure 3.20 See Exercise 3.7.

Chapter 3
Inductance and Capacitance

Questions

If a **DC** current is applied, what is the voltage?

Can the current change *instantly*?

Can the voltage change *instantly*?

How much energy does an inductor dissipate?

Chapter 3
Inductance and Capacitance

Inductance in series and parallel

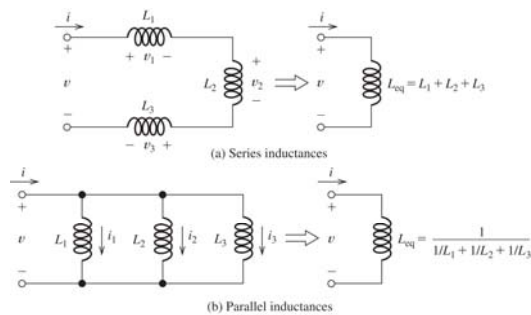


Figure 3.21 Inductances in series and parallel are combined in the same manner as resistances.

Chapter 3
Inductance and Capacitance

Proof for parallel inductance

$$v = L \frac{di}{dt} = L_1 \frac{di_1}{dt} = L_2 \frac{di_2}{dt} = L_3 \frac{di_3}{dt}$$

$$\frac{di}{dt} = \frac{di_1}{dt} + \frac{di_2}{dt} + \frac{di_3}{dt} = \frac{v}{L_1} + \frac{v}{L_2} + \frac{v}{L_3} = \frac{v}{L}$$

$$\frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} = \frac{1}{L}$$

Chapter 3
Inductance and Capacitance

Exercise 3.10: Find equivalent inductance

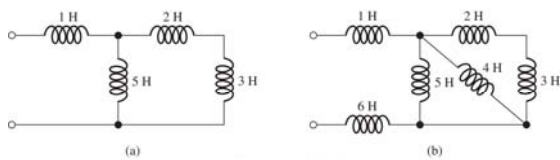


Figure 3.23 See Exercise 3.10.

Chapter 3
Inductance and Capacitance

Real model of **practical** inductors

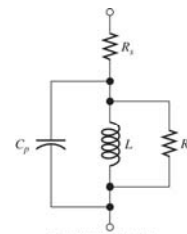


Figure 3.24 Circuit model for real inductors including several parasitic elements.

Chapter 3
Inductance and Capacitance