

I. Current and Kirchhoff's Current Law

- Charge is a fundamental electrical quantity
- Typically denoted by the symbol Q , and its SI unit is the Coulomb (C)
- The smallest amount of charge that exists is the charge that is carried by an electron:

$$Q_e = 1.602 \times 10^{-19} \text{ C}$$

Always include units, otherwise there is no meaning

Current: Free electrons on the move

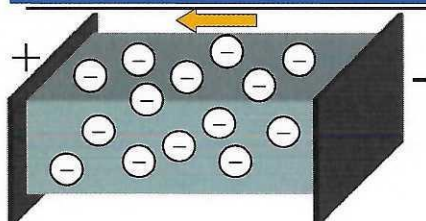


Fig 2a. A voltage is applied to move the charges

Key Concept 1
For current to flow, there must be mobile charges

- Direction of electron flows is from negative to positive
- Direction of current flows (positive charges) is from positive to negative
- Typically denoted by the symbol, I
- SI unit is the Ampere (A)

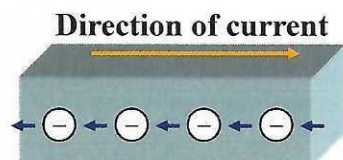


Fig 2b. Movement of electrons gives rise to current

0

Current must run in loops

- If a current flows out of a given point, then it must return to that point with the same amount
- Current must flow in loops
- What goes around comes around

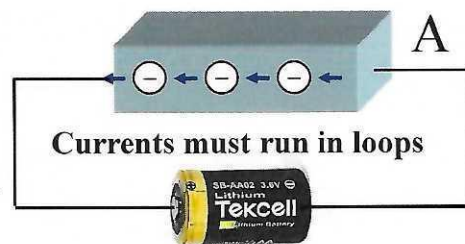


Fig 3. Current must run in loops

Key Concept 2

Currents must run in loops (otherwise charge is either destroyed or created which cannot happen)

Fundamental law for charge

- Current has to flow in closed loop
- No current flows if there is a break in the path
- Underlying physical law: Charge cannot be created or destroyed ("what goes in must also come out")
- This is the basis of Kirchhoff's Current Law

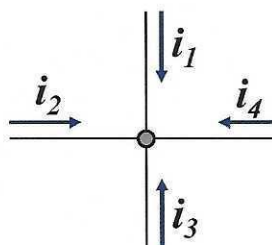


Fig 4.


Kirchhoff's current law

Sum of currents at a node must equal to zero:

$$i_1 + i_2 + i_3 + i_4 = 0$$

Kirchhoff's current law

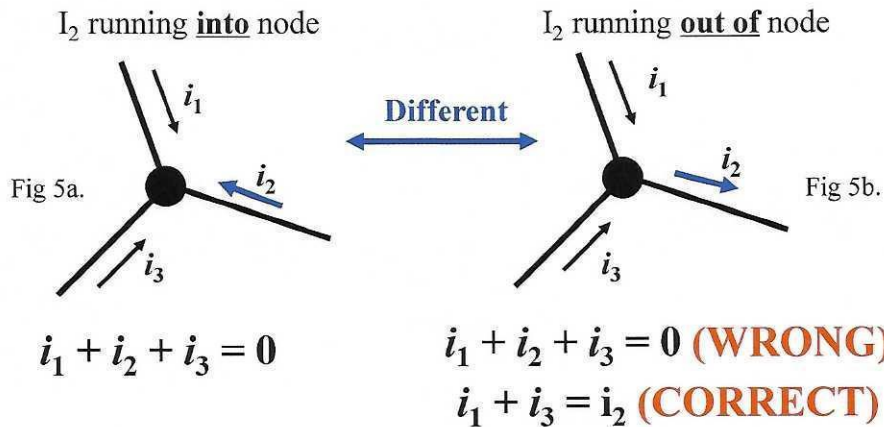Does the direction of current matter? **YES!!**



Block A Unit 1


7

Kirchhoff's current law

Sign convention when applying KCL

Currents flowing IN - Positive

Currents flowing OUT - Negative

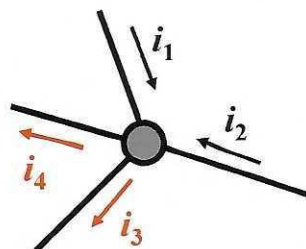

Entering: i_1 & i_2 (+ve)

Exiting: i_3 & i_4 (-ve)

$$i_1 + i_2 - i_3 - i_4 = 0$$


Block A Unit 1

8

Worked Example on KCL

Find the unknown current within each of the following circuit networks

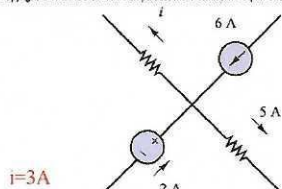
Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



$$-i + 6 - 5 + 2 = 0$$

$$i = 3 \text{ A} \#$$

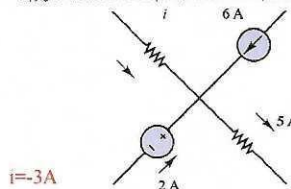Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display




$$i + 6 - 5 + 2 = 0$$

$$i = -3 \text{ A} \#$$


Voltage and Kirchhoff's Voltage Law

- Energy is required to move electrons between 2 points
- This energy could come from the battery cell connected to the circuit
- As the current goes across the cell, energy is pumped in
- As the current goes through a light bulb, energy is consumed
- The amount of energy required to move a unit charge is given by the voltage
- SI unit is Voltage (V)

Potential Difference

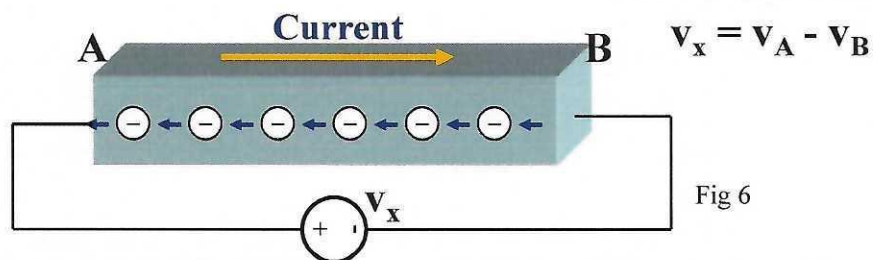

Sign Convention

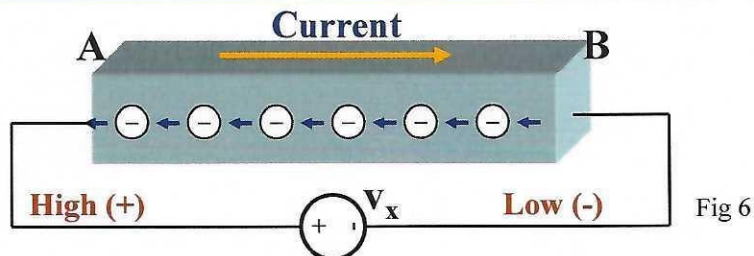

Sign Convention for Voltage

Voltage **risers** (negative to positive) along the direction of the current for an element that is **generating** power

Voltage **drops** (positive to negative) along the direction of the current for an element that is **consuming** power

Kirchhoff's Voltage Law (KVL)

- KVL states that the sum of voltages around a loop must equal to zero
- If a voltage starts at any given point, no gain or loss of any voltage when it returns to the same point
- Whatever energy is pumped into the loop must also be consumed

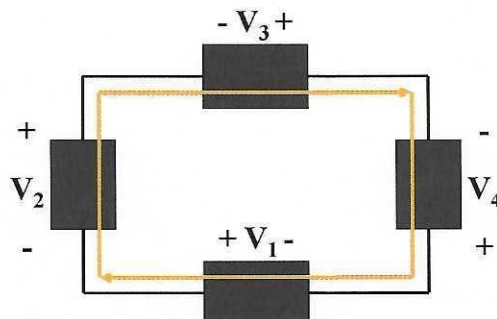


Fig 7: Voltages around a closed loop

Kirchhoff's voltage law

Net voltage around a closed circuit is zero:

$$v_1 + v_2 + v_3 + v_4 = 0$$

Kirchhoff's voltage law

- First, you need to define the direction
 - V_1 and V_3 are voltage rises (positive) while V_2 is a voltage drop (negative)
 - In the other direction, V_2 is voltage rise (positive), while V_1 and V_3 are voltage drops (negative)
- $$V_2 - V_1 - V_3 = 0$$

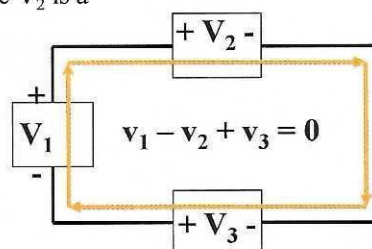


Fig 8: Defined voltage drops and rises


Sign Convention for KVL
 Voltage RISE – Positive
 Voltage DROP – Negative

Worked Example on KVL

Apply KVL to find voltage V_1 and V_2

$$V_1 = 12V, V_2 = 2V$$

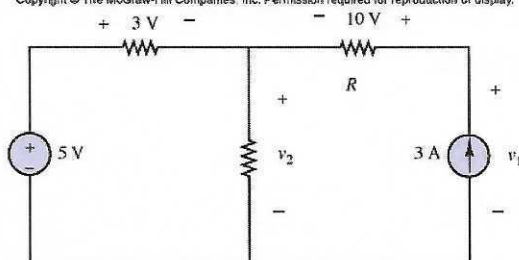Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



$$\begin{aligned} V_1 &= \\ 5 - 3 + 10 - V_1 &= 0 \\ V_1 &= 12V \# \end{aligned}$$

$$\begin{aligned} V_2 &= \\ 5 - 3 - V_2 &= 0 \\ V_2 &= 2V \# \end{aligned}$$

II. Resistance and Ohm's Law

- When current flows through a conductor, it will always experience some resistance
- Resistance is given by the change in voltage over change in current
- SI unit is Ohm (Ω)
- If the voltage is linear with current, then resistance is said to be linear and obeys Ohm's law

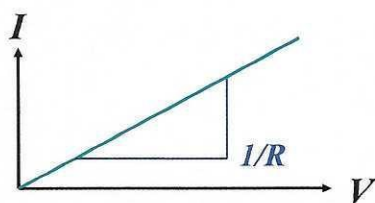


Fig 9a: Linear resistance that obeys Ohm's law

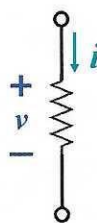


Fig 9b

Ohm's law is given as:

$$V = IR$$


Important point to note:

If an unknown current is defined to flow from A to B, the voltage at A is assumed to be higher than B.

Worked Example Applying 3 Laws

Find the current through the 15Ω resistor $I_1 = 6.67\text{A}, I_2 = 3.33\text{A}$

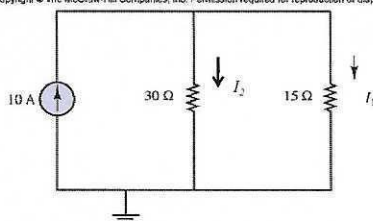Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



KCL:

$$10 - I_2 - I_1 = 0 \quad \text{--- (1)}$$

30-Ω & 15-Ω resistors have same voltage

$$I_2 \cdot 30 = I_1 \cdot 15$$

$$I_1 = 2I_2 \quad \text{--- (2)}$$

From (1) & (2)

$$I_1 = 6.67\text{A}$$

$$I_2 = 3.33\text{A}$$

III. Electrical Power

- A voltage drop in the direction of the current indicates the power is consumed
- Conversely, a voltage rise in the direction of the current indicates that power is generated
- If the voltage across a resistor is V , and current through it is I , then the power consumed is given by:

$$P = VI$$

$$\text{Ohm's law} \rightarrow P = I^2 R$$

$$\text{Ohm's law} \rightarrow P = V^2 / R$$

Power generated by source

MUST EQUAL

Power dissipated in the load


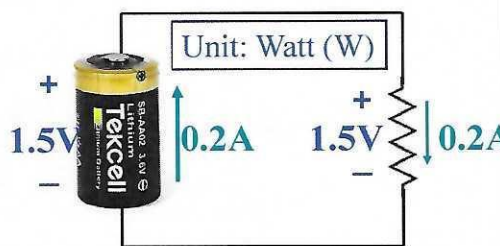


Fig 10: Power generated and consumed in a circuit

Worked Example on Power

Determine which components are absorbing power and which are delivering power

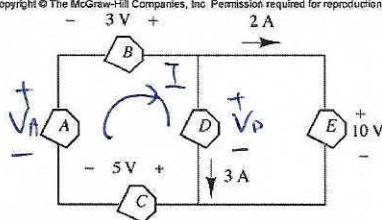Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



Delivering: A (60W), B (15W)
Consuming: C (25W), D (30W), E (20W)

To find V_A (consider outer loop)

$$V_A + 3 - 10 - 5 = 0$$

$$V_A = +12V, P_A = V_A \cdot I_A = 12 \times (2A + 3A)$$

To find V_D

Consider the right loop: $10 - V_D = 0$

$$V_D = 10V$$


$$P_D = V_D I_D = 10 \times 3$$

$$\Rightarrow P_D = 30W \text{ (consuming power)}$$

Consuming power because the current flows into $+V_D$ voltage

$\Rightarrow P_A = 60W$ (delivering power)
delivering power because the current is leaving $+V_A$ voltage.

Terminology: Branch and Node

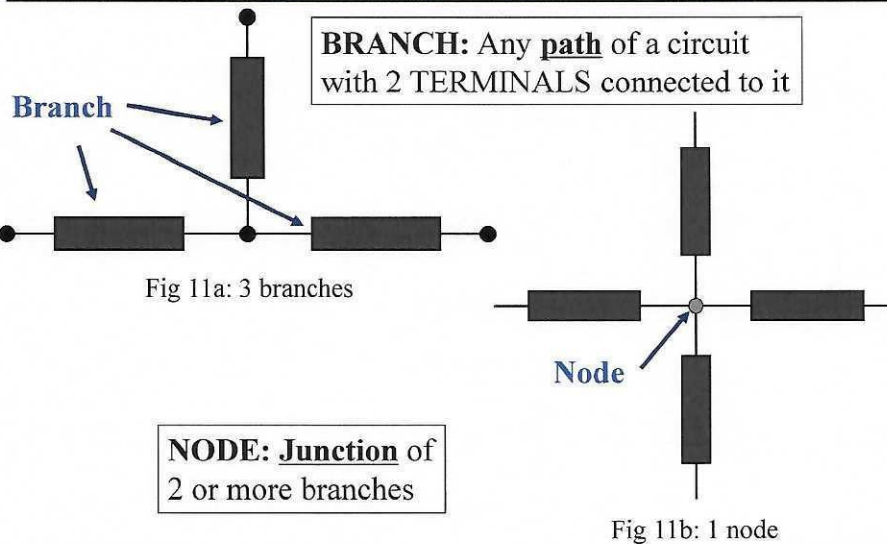

Terminology: Loop and Mesh

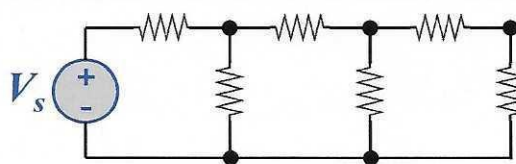


Fig 12: Loops (6) and meshes (3)

- **Loop:** Any closed connection of branches
- **Mesh:** Loop that does not contain any loops
- In Fig 12, there are 6 loops and 3 meshes.
- We will use the term mesh more than loop in this course

IV. Sources, Short Circuit and Open Circuit

- Loads (e.g. resistors) consume power
- Sources on the other hand deliver power

Ideal Voltage Source

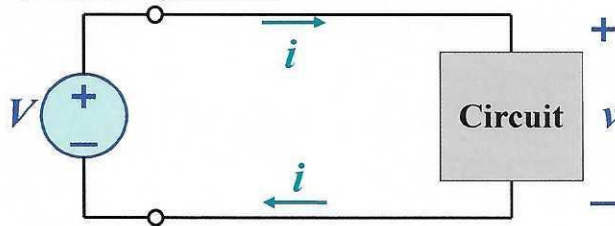


Fig 13a: Ideal voltage source in a circuit

- The purpose of a voltage source is to keep the voltage across its terminals unchanged
- Current through a voltage source is allowed to change in order to maintain the voltage at V with reference to Fig 13a (i.e., a different i for a different circuit loading)

Ideal Current Source

Ideal Current Source

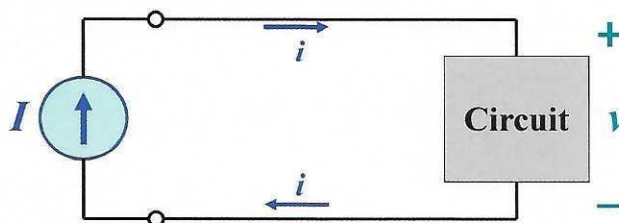


Fig 13b: Ideal current source in a circuit

- The purpose of a current source is to keep the current flowing through it unchanged
- Voltage across a current source is allowed to change in order to maintain the current at I with reference to Fig 13b

Recognize the differences between an ideal voltage and current source in their functions and symbols.

Short Circuit

- A short circuit means connecting 2 or more terminals together so that the voltage between them is zero
- It is typically associated with currents rather than voltage, e.g. short circuit current

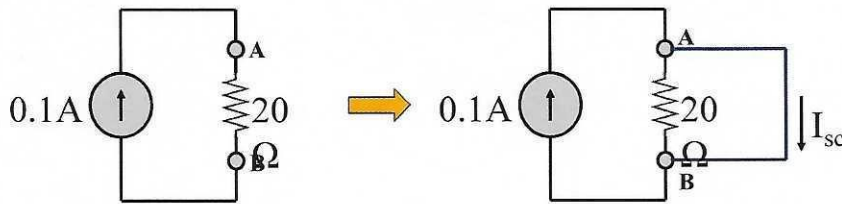


Fig 14a: Short circuiting the resistor

- All the current from the source flows through the short circuit, bypassing the resistor
- Short circuit current $I_{sc} = 0.1 \text{ A}$

Open Circuit

- A open circuit means no extra connections are imposed across two terminals
- It is typically associated with voltage rather than current, e.g. open circuit voltage


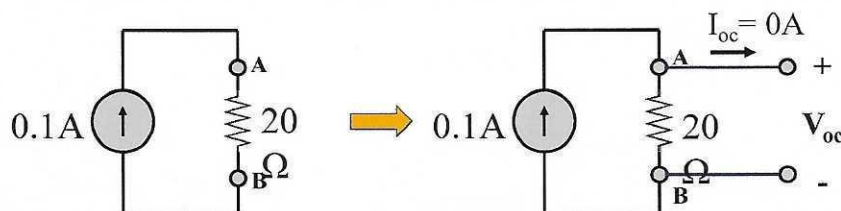



Fig 14b: Open circuiting the resistor

- In Fig 14b, the open circuit voltage of the resistor is simply the voltage across the resistor
- Open circuit Voltage $V_{oc} = 2 \text{ V}$

Self-contradictory circuits

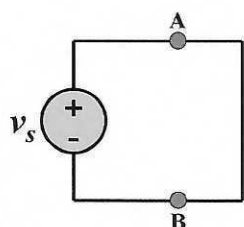

What is the voltage across A and B?

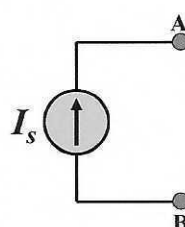

What is the current through the source?

Prefixes

- As engineers, it is important that we replace exponents with prefixes
- For example:
 $0.00215 \text{ A} \rightarrow 2.15 \text{ mA}$
 never $2.15 \times 10^{-3} \text{ A}$
- Make sure you memorize the prefixes from nano (n) to mega (M)

Prefixes: Memorize and apply them!


tera	T	10^{12}
giga	G	10^9
mega	M	10^6
kilo	k	10^3
milli	m	10^{-3}
micro	μ	10^{-6}
nano	n	10^{-9}
pico	p	10^{-12}
femto	f	10^{-15}

V. Resistive Networks

- Resistors are either arranged in parallel or in series or as combination of both

Parallel Network

Fig 15a: Parallel resistive network

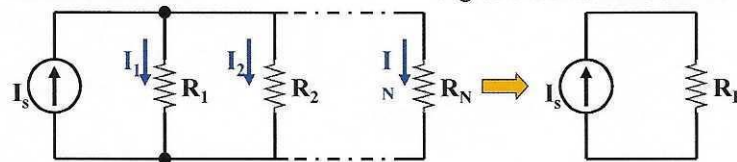

Equivalent Resistance R_p :
$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_N}$$

Current Divider Rule

$$I_k = \frac{R_p}{R_k} I_s$$


- Current (I_s) from the source will have to be shared between the resistors (R_k) in each branch

Proof: $I_s = I_1 + I_2 + I_3 + \dots + I_N \Rightarrow \frac{V}{R_p} = \frac{V}{R_1} + \frac{V}{R_2} + \dots + \frac{V}{R_N}$
 $\Rightarrow \frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}$

Series network (Highlights)

Series Network

Fig 15b: Series resistive network

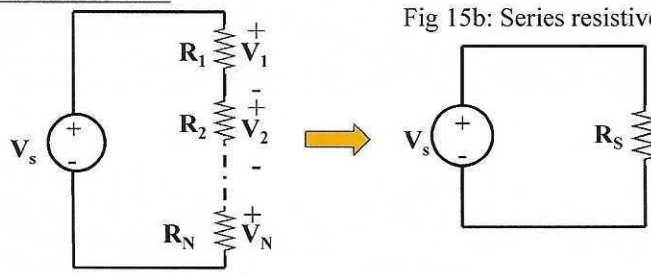

Equivalent Resistance R_p :

$$R_s = R_1 + R_2 + \dots + R_N$$

Voltage Divider Rule


$$V_k = \frac{R_k}{R_s} V_s$$

- Total voltage drop across all the resistors (V_s) in series is the sum total of voltage (V_k) drops across each resistor

Worked Example on Current Divider Rule

Rank the currents from largest to smallest if $R_2 > R_4 > R_1 > R_5 > R_3$

$$I_1 > I_5 > I_1 > I_4 > I_2$$

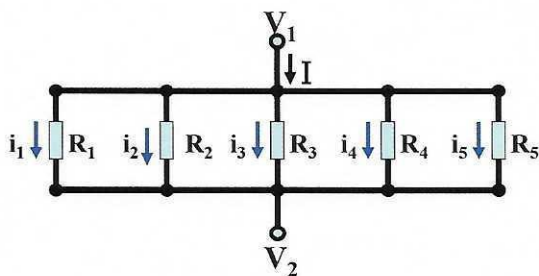


Worked Example on Voltage Divider Rule

Rank the potential difference from largest to smallest

if $R_2 > R_4 > R_1 > R_5 > R_3$


$$V_2 > V_4 > V_1 > V_5 > V_3$$

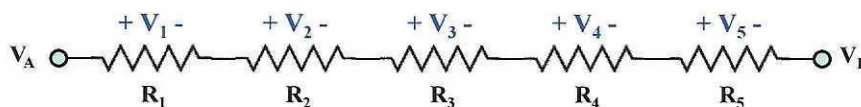

Worked Example 1 on Resistive Networks

Find the effective resistance across A and B
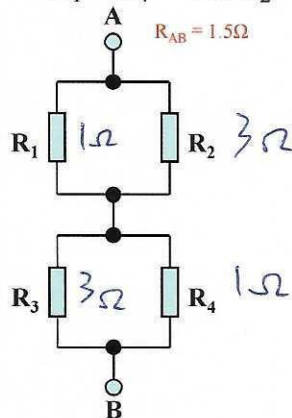
$$R_1 = R_4 = 1\Omega, R_2 = R_3 = 3\Omega$$




$$R_{AB} = 1.5\Omega$$

$$R_{AB} = R_1 \parallel R_2 + R_3 \parallel R_4$$

$$= \frac{R_1 R_2}{R_1 + R_2} \times 2$$

$$= \frac{1 \times 3}{1 + 3} \times 2$$

$$R_{AB} = 1.5\Omega$$

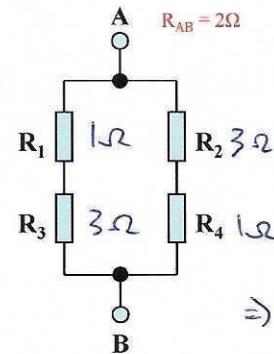

$$R_{AB} = 2\Omega$$

$$R_{AB} = (R_1 + R_3) \parallel (R_2 + R_4)$$

$$= 4 \parallel 4$$

$$= \frac{4 \times 4}{4 + 4}$$



$$\Rightarrow R_{AB} = 2\Omega$$

Worked Example 2 on Resistive Networks

What is the equivalent resistance seen by the source?

What is power supplied by the source?

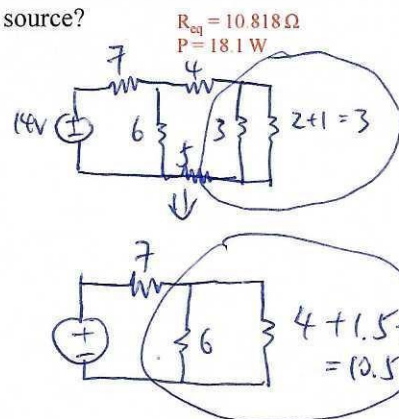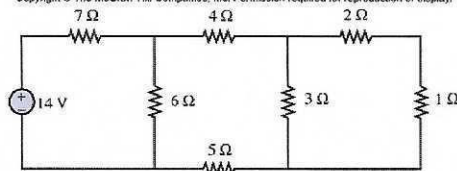Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



$$R_{eq} = 10.818\Omega$$

$$P = 18.1\text{ W}$$

$$\Rightarrow 3 \parallel 3$$

$$= \frac{3 \times 3}{3 + 3}$$

$$= 1.5\Omega$$

$$\Rightarrow \frac{6 \times 10.5}{6 + 10.5}$$

$$= \frac{6 \times 10.5}{16.5}$$

$$= 3.818\Omega$$

$$R_{eq} = 7 + 3.818 = 10.818\Omega$$

$$P = \frac{V^2}{R_{eq}} = \frac{14^2}{10.818} = 18.1\text{ W}$$

VI. Measuring Instruments - Voltmeter

- Voltmeter measures voltage across a circuit element

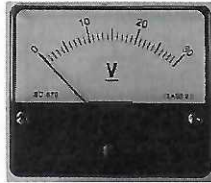


Fig 16: Image of typical voltage with a measuring range up to 30V

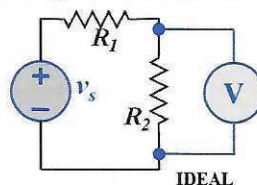


Fig 17a: Placement of an ideal voltmeter to measure the PD across R_2

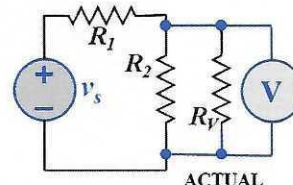


Fig 17b: Circuit model of how a real voltmeter behaves, which looks like a large parallel resistor (R_v)

How would you place the voltmeter in the circuits?

- Connected in **parallel** with the element being measured

In Fig 17a, voltmeter has no effect on original circuit.

In Fig 17b, voltmeter will steal current from R_2 . This will change the voltage measured across R_2 . **Thus, the PD measured with a voltmeter is lower than the true value.**

Worked Example on Voltmeters

Referring to Fig 17b, if $V_s = 5V$, and $R_v = 1M\Omega$, find the voltage across R_2 when

(i) $R_1 = R_2 = 1k\Omega$ $V = 2.5V$

(ii) $R_1 = R_2 = 1M\Omega$ $V = 1.67V$

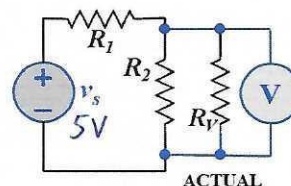


Fig 17b

(i) $R_1 = R_2 = 1k, R_v = 1M = 1000k$

$$R_p = R_2 \parallel R_v = \frac{1 \times 1000}{1 + 1000} \approx 1k$$

$$V_{R_2} = \frac{R_p}{R_1 + R_p} \times V_s = \frac{1}{1 + 1} \times 5 = 2.5V \#$$

(ii) $R_1 = R_2 = 1M, R_v = 1M$

$$R_p = R_2 \parallel R_v = \frac{1 \times 1}{1 + 1} = 0.5M$$

$$V_{R_2} = \frac{R_p}{R_1 + R_p} V_s = \frac{0.5}{1 + 0.5} \times 5 = 1.67V \#$$

Ammeter

- Ammeter measures current



Fig 18: Image of typical current with a measuring range up to 20A

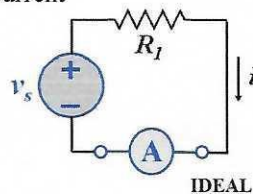


Fig 19a: Placement of an ideal ammeter to measure current through R_1

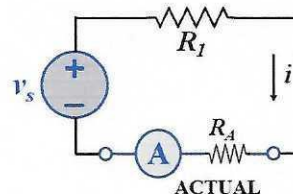


Fig 19b: Circuit model of how a real ammeter behaves, which looks like a small series resistor (R_A)

How would you place the ammeter in the circuits?

- Connected in series with the element being measured

In Fig 19a, ammeter has no effect on original circuit.

In Fig 19b, ammeter contains some resistance (R_A), adding to the total resistance, lowering the measured current. **Thus, the current measured with an ammeter is lower than the true value.**

Ammeter Example

Referring to Fig 19b, if $V_s = 5V$, and $R_A = 1\Omega$, find the loop current when

- (i) $R_1 = 1k\Omega$ $I = 4.995 \text{ mA}$
 (ii) $R_1 = 2\Omega$ $I = 1.67A$

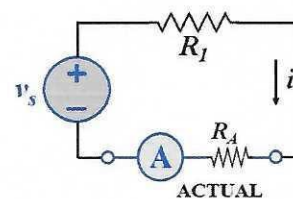


Fig 19b

(i) $R_1 = 1k\Omega$

$$I = \frac{5}{1 + 10^{-3}} = \frac{5}{1.001} = 4.995 \text{ A} \neq$$

(ii) $R_1 = 2\Omega$

$$I = \frac{5}{1 + 2} = \frac{5}{3} = 1.67 \text{ A} \neq$$