

Review: Chapter 14

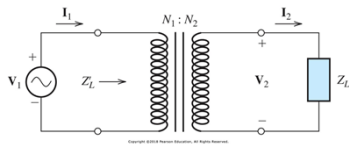


Figure 14.25 The impedance seen looking into the primary is $Z'_L = (N_1 / N_2)^2 \times Z_L$.

$$v_2(t) = \frac{N_2}{N_1} v_1(t) \quad i_2(t) = \frac{N_1}{N_2} i_1(t)$$

$$p_2(t) = p_1(t)$$

Chapter 9
Diodes

Chapter 9 Diodes

1. Diode operation principle.
2. Voltage regulator
3. Rectifier
4. Wave shaping circuits

Chapter 9
Diodes

Basic diode concept

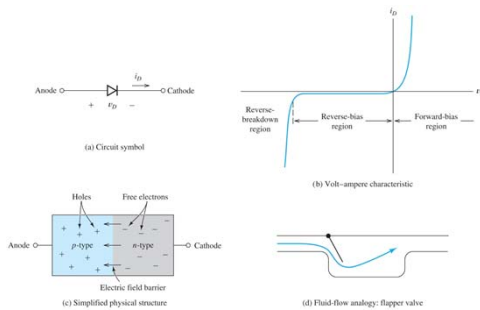


Figure 9.1 Semiconductor diode.

Chapter 9
Diodes

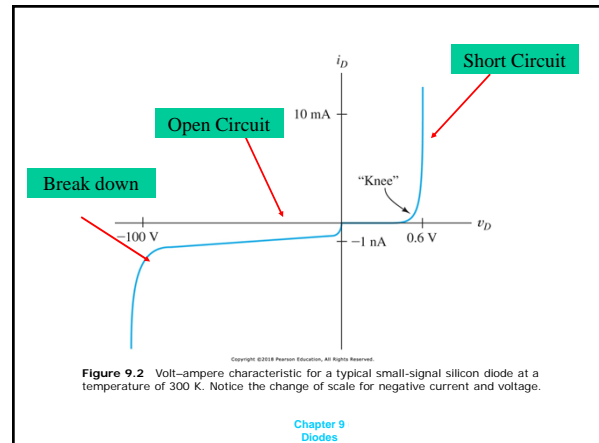


Figure 9.2 Volt-ampere characteristic for a typical small-signal silicon diode at a temperature of 300 K. Notice the change of scale for negative current and voltage.

Chapter 9
Diodes

Shockley Equation

$$i_D = I_s \left[\exp\left(\frac{v_D}{nV_T}\right) - 1 \right]$$

I_s : Saturation current

n : Emission coefficient

$$V_T = \frac{kT}{q}$$

$k = 1.38 \times 10^{-23}$ J/K: Boltzmann's constant
 $q = 1.60 \times 10^{-19}$ C: the electrical charge of an electron.
 At a temperature of 300 K, we have $V_T \cong 26$ mV

Chapter 9
Diodes

Zener Diodes


Diodes that are intended to operate in the breakdown region are called **Zener diodes**.



Chapter 9
Diodes

Zener-diode voltage-regulator circuits

A voltage regulator circuit provides a nearly **constant** voltage to a load from a **variable** source.

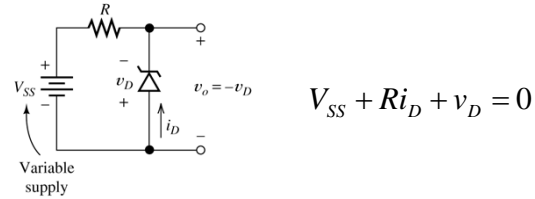

Chapter 9
Diodes

Ideal-diode model

The ideal diode acts as a **short circuit** for forward currents and as an **open circuit** with reverse voltage applied.

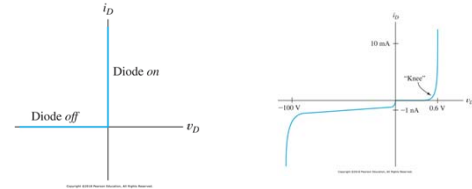


Figure 9.15 Ideal-diode volt-ampere characteristic.

Chapter 9
Diodes

Diode circuit analysis

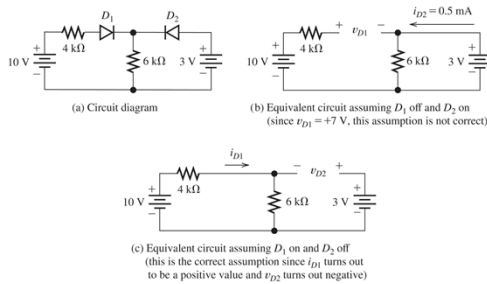


Figure 9.16 Analysis of a diode circuit, using the ideal-diode model. See Example 9.5.

Chapter 9
Diodes

Exercise 9.8 Find the diode states

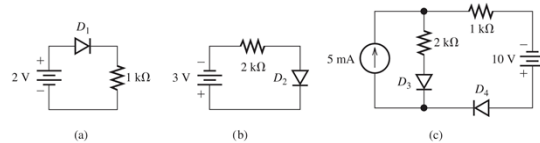


Figure 9.17 Circuits for Exercise 9.8.

Chapter 9
Diodes

Simple diode model

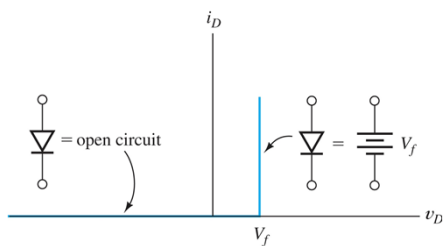


Figure 9.23 Simple piecewise-linear equivalent for the diode.

Chapter 9
Diodes

Application: Half-wave rectifier

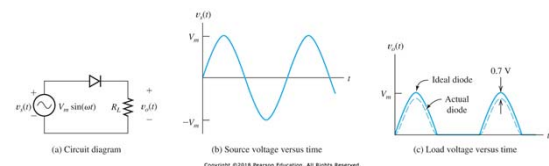


Figure 9.24 Half-wave rectifier with resistive load.

Chapter 9
Diodes

Application: Battery charge circuit

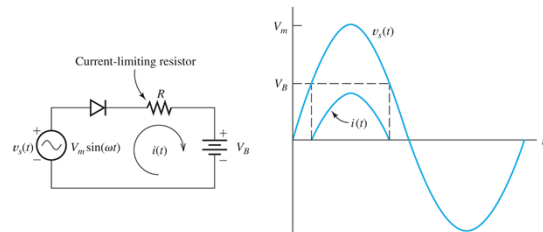


Figure 9.25 Half-wave rectifier used to charge a battery.

Chapter 9
Diodes

Half-wave rectifier with smoothing capacitor

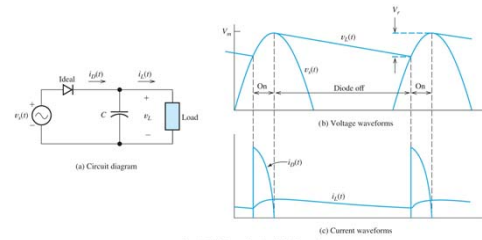


Figure 9.26 Half-wave rectifier with smoothing capacitor.

$$C = \frac{I_L T}{V_r} \quad V_L \cong V_m - \frac{V_r}{2}$$

Chapter 9
Diodes

Full-wave rectifier

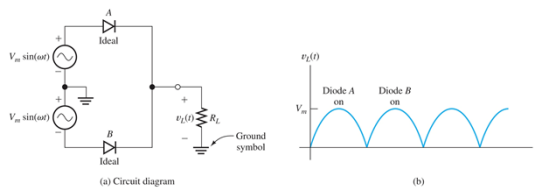


Figure 9.27 Full-wave rectifier.

Chapter 9
Diodes

Full-wave rectifier

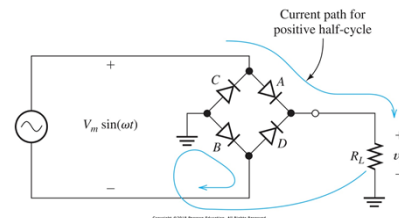


Figure 9.28 Diode-bridge full-wave rectifier.

Chapter 9
Diodes

Peak Inverse Voltage

An important aspect of rectifier circuits is the **peak inverse voltage** (PIV) across the diodes.

Smoothing capacitor:

The capacitance required for a full-wave rectifier is given by:

$$C = \frac{I_L T}{2V_r}$$

Chapter 9
Diodes

Application: Clipper circuits


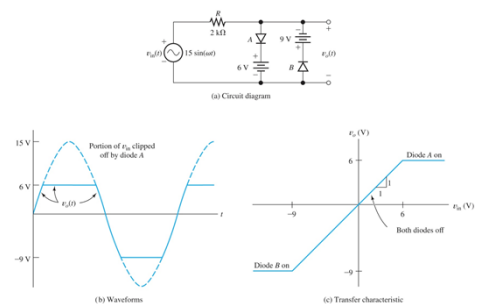


Figure 9.29 Clipper circuit.

Chapter 9
Diodes

Clipper circuits

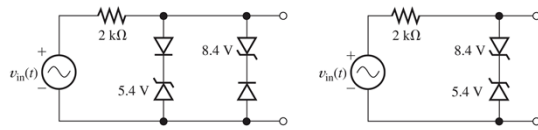

(a) Circuit of Figure 9.29 with batteries replaced by Zener diodes and allowance made for a 0.6-V forward diode drop



(b) Simpler circuit

Copyright © 2013 Pearson Education, All Rights Reserved.


Figure 9.30 Circuits with nearly the same performance as the circuit of Figure 9.29.

Chapter 9
Diodes

Exercise 9.15

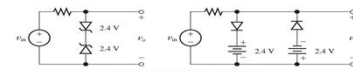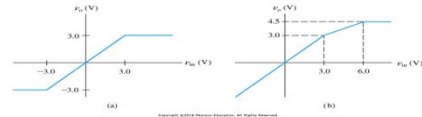

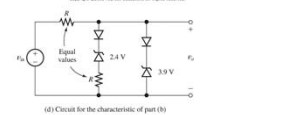(c) Circuits for the characteristic of part (a)



(d) Circuit for the characteristic of part (b)

Figure 9.32 See Exercise 9.15.

Chapter 9
Diodes