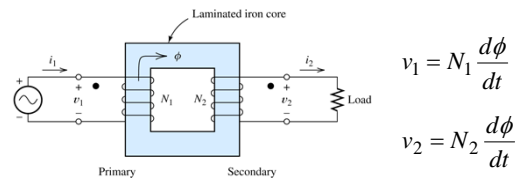


## Chapter 14 Transformers

1. Ideal transformers and their functions.
2. Real transformers: equivalent circuits, regulations and power efficiencies.

Chapter 14  
Magnetic Circuits and Transformers

### Ideal Transformers



$$v_2(t) = \frac{N_2}{N_1} v_1(t) \quad i_2(t) = \frac{N_1}{N_2} i_1(t)$$

$$p_2(t) = p_1(t)$$

Chapter 14  
Magnetic Circuits and Transformers

### Symbol and analog

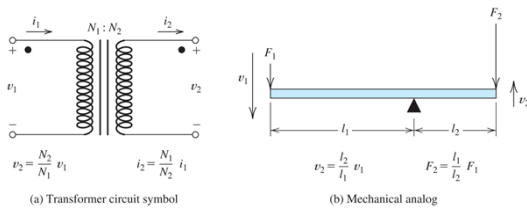


Figure 14.23 The circuit symbol for a transformer and its mechanical analog.

Chapter 14  
Magnetic Circuits and Transformers

### Example 14.10

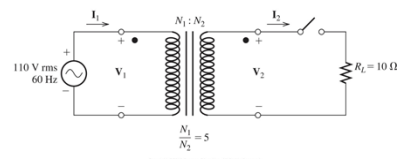


Figure 14.24 Circuit of Example 14.10.

$$V_{2rms} = \frac{N_2}{N_1} V_{1rms} = \frac{1}{5} \times 110 = 22V$$

Chapter 14  
Magnetic Circuits and Transformers

### Impedance Transformations

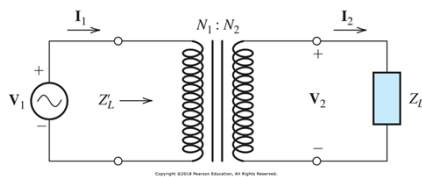


Figure 14.25 The impedance seen looking into the primary is  $Z'_L = (N_1 / N_2)^2 \times Z_L$ .

$$Z'_L = \frac{V_1}{I_1} = \left( \frac{N_1}{N_2} \right)^2 Z_L$$

Chapter 14  
Magnetic Circuits and Transformers

### Example 14.11

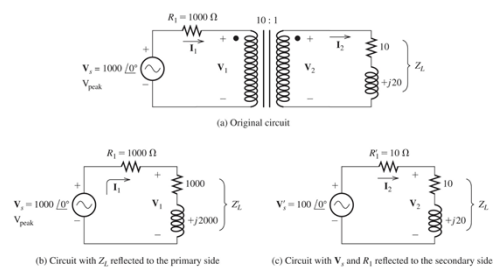


Figure 14.26 The circuit of Examples 15.11 and 15.12.

Chapter 14  
Magnetic Circuits and Transformers

$$Z_L' = \left( \frac{N_1}{N_2} \right)^2 Z_L = 10^2 (10 + j20) = 1000 + j2000$$

$$Z_s = R_1 + Z_L' = 2000 + j2000 = 2828 \angle 45^\circ$$

$$I_1 = \frac{V_s}{Z_s} = 0.3536 \angle -45^\circ$$

$$V_1 = I_1 Z_L' = 790.6 \angle 18.43^\circ$$

$$I_2 = \frac{N_1}{N_2} I_1 = 3.536 \angle -45^\circ$$

Chapter 14  
Magnetic Circuits and Transformers

### Exercise 14.18: find the turn ratio for maximum power delivery


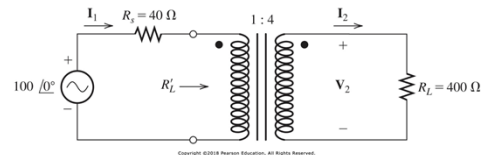


Figure 14.27 Circuit of Exercises 15.16 and 15.17.

Chapter 14  
Magnetic Circuits and Transformers

## Real Transformers

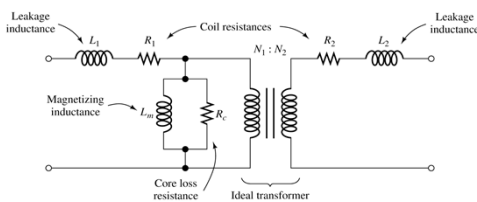

Chapter 14  
Magnetic Circuits and Transformers

## Variations of the Transformer Model

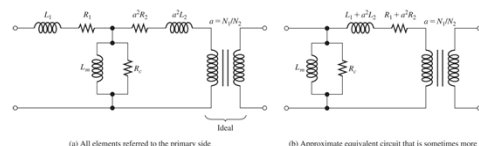


Figure 14.29 Variations of the transformer equivalent circuit. The circuit of (b) is not exactly equivalent to that of (a), but is sufficiently accurate for practical applications.

Chapter 14  
Magnetic Circuits and Transformers

**Table 14.1** Circuit Values of a 60-Hz 20-kVA 2400/240-V Transformer Compared with Those of an Ideal Transformer

Element Name	Symbol	Ideal	Real
Primary resistance	$R_1$	0	3.0 $\Omega$
Secondary resistance	$R_2$	0	0.03 $\Omega$
Primary leakage reactance	$X_1 = \omega L_1$	0	6.5 $\Omega$
Secondary leakage reactance	$X_2 = \omega L_2$	0	0.07 $\Omega$
Magnetizing reactance	$X_m = \omega L_m$	$\infty$	15 k $\Omega$
Core-loss resistance	$R_c$	$\infty$	100 k $\Omega$

Copyright © 2018 Pearson Education, All Rights Reserved.

Chapter 14  
Magnetic Circuits and Transformers

## Regulation and Efficiency

$$\text{percent regulation} = \frac{V_{\text{no-load}} - V_{\text{load}}}{V_{\text{load}}} \times 100\%$$

$$\text{power efficiency} = \frac{P_{\text{load}}}{P_{\text{in}}} \times 100\% = \left( 1 - \frac{P_{\text{loss}}}{P_{\text{in}}} \right) \times 100\%$$

Chapter 14  
Magnetic Circuits and Transformers

### Example 14.13

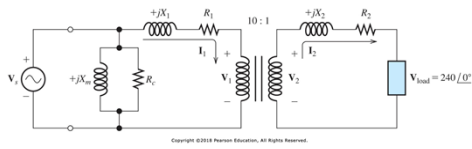


Figure 14.30 Circuit of Example 14.13.

$$V_{load} = 240 \angle 0^\circ V, \quad P_{app} = 20 \text{ kVA}$$

Chapter 14  
Magnetic Circuits and Transformers

$$I_2 = 83.33 \angle -36.87^\circ A$$

$$I_1 = \frac{N_2}{N_1} I_2 = 8.333 \angle -36.87^\circ A$$

$$V_2 = V_{load} + I_2(R_2 + jX_2) = 245.50 + j3.166 A$$

$$V_1 = \frac{N_1}{N_2} V_2 = 2455 + j31.66 V$$

Chapter 14  
Magnetic Circuits and Transformers

$$P_{in} = P_{load} + P_{loss} = 16479.5 W$$

$$efficiency = (1 - \frac{P_{loss}}{P_{in}}) \times 100\% = 97.09\%$$

No-load  
case:

$$I_1 = I_2 = 0$$

$$V_1 = V_s = 2508.2 V$$

Chapter 14  
Magnetic Circuits and Transformers