

**Part II: Written Questions (Total 60 minutes; 3 questions)**

**Question 1 (10 points, 12 minutes)**

It is known that  $i_1 = \frac{1}{2}i_0$ , and  $v_1 = 3v_2$  in the following circuit.

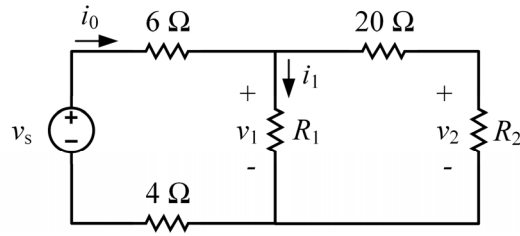


Fig. Q1

(1) Determine the values of  $R_1$ , and  $R_2$ . **(6 points)**

(2) If  $i_1 = 0.8$  A, find the power supplied by the voltage source. **(4 points)**

**Question 2 (18 points, 22 minutes)**

A circuit is given in Fig. Q2.

(1) If  $R_1 = 4 \Omega$  and  $R_2 = 2 \Omega$ , find the current  $i$  and voltage  $v$ ; **(5 points)**

(2) If  $i = 2$  A and  $v = 36$  V, find the resistances  $R_1$  and  $R_2$ ; **(5 points)**

(3) Suppose the voltage and current sources supply powers of 36 W and 90 W, respectively, find the current  $i$ , voltage  $v$ , and resistances  $R_1$  and  $R_2$ . **(8 points)**

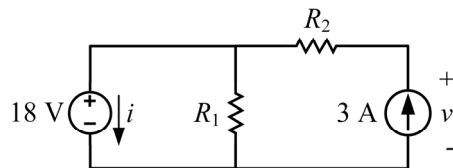


Fig. Q2

**Question 3 (22 points, 26 minutes)**

The following circuit has two parts: the 'Source' and 'load' parts.

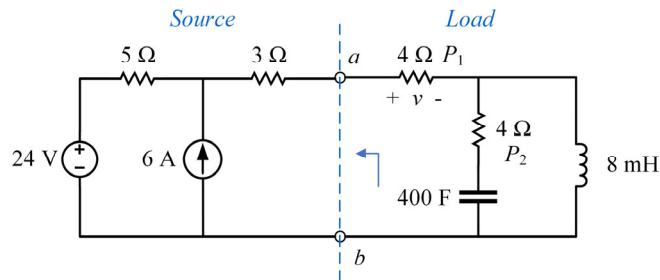


Fig. Q3a

- (1) Find the Thevenin equivalent circuit looking into the 'source' part from the terminals  $a$ - $b$  in Fig. Q3a; **(4 points)**
- (2) Find the voltage  $v$  and powers  $P_1$  and  $P_2$  consumed by the two  $4\text{-}\Omega$  resistors in Fig. Q3a; **(6 points)**
- (3) If the 'load' part is replaced by a resistor  $R$  in Fig. Q3b, find the resistance of  $R$  that will consume the maximum power  $P_{\max}$  and the value of the corresponding  $P_{\max}$ ; and **(6 points)**
- (4) If the 'load' part is replaced by a current-controlled voltage source as shown in Fig. Q3c, find the current  $i$ . **(6 points)**

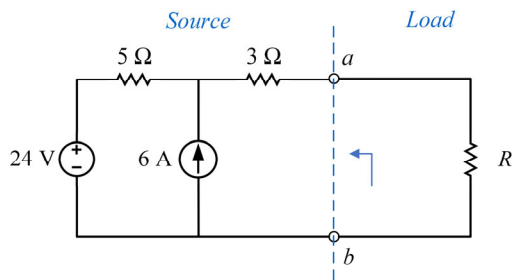


Fig. Q3b


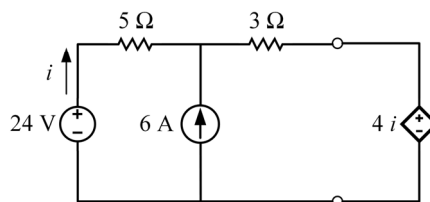


Fig. Q3c

**Solution:**

**Q1**

(1)

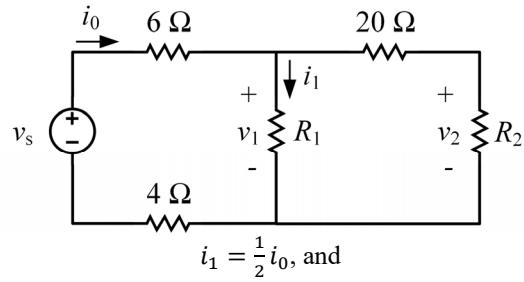

Given by

$$v_1 = v_{20\Omega} + v_2$$

$$v_1 = 3v_2$$

$$v_{20\Omega} = 2v_2$$

Based on voltage division

$$R_2 = \frac{1}{2} R_{20\Omega} = 10\Omega$$

Given by

$$i_1 = \frac{1}{2} i_0$$

Based on Current division

$$R_1 = R_{20\Omega} + R_2 = 30\Omega$$

(2)


$$i_1 = 0.8\text{ A}$$

$$i_0 = 2i_1 = 1.6\text{ A}$$

$$R_{eq} = 6\Omega + 4\Omega + (R_1 || (R_{20\Omega} + R_2)) = 25\Omega$$

$$P = I^2 R_{eq} = 64\text{ W}$$

**Q2**

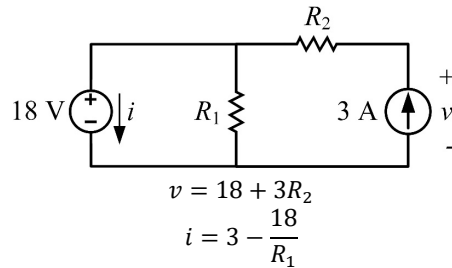

(1)

$$v = 24\text{ V}, i = -1.5\text{ A}.$$

(2)

$$R_1 = 18\Omega, R_2 = 6\Omega$$

(3)

$$i = -36/18 = -2\text{ A}, v = 90/3 = 30\text{ V}$$

Then

$$R_1 = 3.6\Omega, R_2 = 4\Omega$$

**Q3**

(1)

$$R_{ab} = 8\Omega$$

When the current source is killed,  $U_{ab1} = 24\text{ V}$ .

When the voltage source is killed,

$$I_N = 6 \times \frac{5}{8} = \frac{15}{4}\text{ A}$$

$$\therefore U_{ab2} = 8 \times \frac{15}{4} = 30\text{ V}$$

$$\therefore U_{ab} = U_{ab1} + U_{ab2} = 54\text{ V}$$

(2)

Since this is a DC circuit, therefore the capacitor opens the circuit, and the inductor is regarded as a short line.

Thus,  $P_2 = 0$ .

Set  $I$  is the current through the resistor  $4\ \Omega$  whose power is  $P_1 = 0\ \text{W}$

$$I = \frac{54}{8 + 4} = 4.5\ \text{A}$$

$$P_1 = I^2 R = 4.5^2 \times 4 = 81\ \text{W}$$

(3)

The maximum power will be obtained when the load equals to the  $R_{\text{th}}$ , say  $R = R_{\text{th}} = 8\ \Omega$ .

$$\text{Therefore, } P_{\text{max}} = \frac{54^2}{R_{\text{ab}} + R} \times \frac{1}{2} = 91.125\ \text{W}$$

(4)

Set the current inside the first mesh and second mesh are  $I_1$  and  $I_2$ , respectively.

Then,  $i = I_1$

$$\begin{cases} 24 = 5I_1 + 3I_2 + 4I_1 \\ I_2 - I_1 = 6\ \text{A} \end{cases} \rightarrow i = I_1 = 0.5\ \text{A}$$