

Department of Biomedical Engineering

Electrical and Electronic Principles

Gary FENG

Office: Y6721

Tel Ext: 5900


Chapter 1
Introduction

Discovery-Enriched Curriculum (DEC)



Attitude

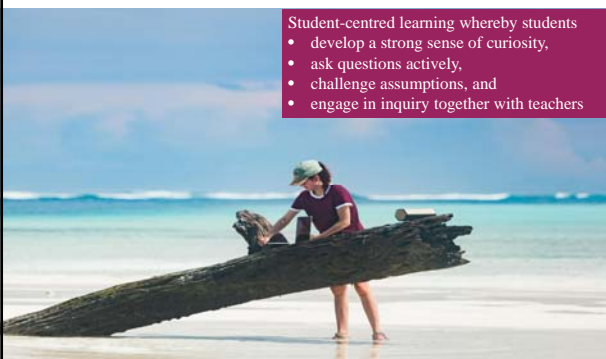Develop an attitude of discovery/innovation/creativity



Ability

Develop the ability/skill needed to discover/innovate/create



Accomplishments

Demonstrate accomplishments of discovery/innovation/creativity



Learning Tips

- Pre-study lecture notes and relevant chapters of the textbook before each lecture
- Identify difficult parts and thus pay more attention to those parts during lecture
- Nurture self-learning capability
- Try to solve as many problems as possible with different approaches
- Try Practice Test from relevant chapters
- Read other reference books if possible

Chapter 1
Introduction

Chapter 1 Introduction

1. Reasons for studying electrical engineering
2. Definitions: current, voltage, and power
3. Circuit elements
4. Basic circuit laws

Chapter 1
Introduction

Overview of Electrical Engineering

Table 1.1 Current and Emerging Electronic/Electrical Applications in Automobiles and Trucks

Safety

Antiskid brakes
Inflatable restraints
Collision warning and avoidance
Blind-zone vehicle detection (especially for large trucks)
Infrared night vision systems
Heads-up displays
Automatic accident notification
Rear-view cameras

Communications and entertainment

AM/FM radio
Digital audio broadcasting
CD/DVD player
Cellular phone
Computer/e-mail
Satellite radio



Copyright ©2014 Pearson Education, All Rights Reserved.

Chapter 1
Introduction

Overview of Electrical Engineering

Table 1.1 Current and Emerging Electronic/Electrical Applications in Automobiles and Trucks

Convenience

Electronic GPS navigation
Personalized seat/mirror/radio settings
Electronic door locks

Emissions, performance, and fuel economy

Vehicle instrumentation
Electronic ignition
Tire inflation sensors
Computerized performance evaluation and maintenance scheduling
Adaptable suspension systems

Alternative propulsion systems

Electric vehicles
Advanced batteries
Hybrid vehicles

Copyright ©2014 Pearson Education, All Rights Reserved.

Chapter 1
Introduction

Biomedical Equipment and Devices



Chapter 1
Introduction

Subdivisions of Electrical Engineering

1. Communication Systems
2. Computers
3. Control Systems
4. Electromagnetics
5. Electronics
6. Photonics
7. Power Systems
8. Signal Processing


Chapter 1
Introduction

Why Study Electrical Engineering?


- To pass the *Fundamentals of Engineering (FE) Examination* as a first step in becoming a *Registered Professional Engineer*
- To have a broad knowledge so that you can lead design projects in your own field
- To be able to operate and maintain electrical systems
- To communicate with electrical engineering consultants

Chapter 1
Introduction

Example of Circuit

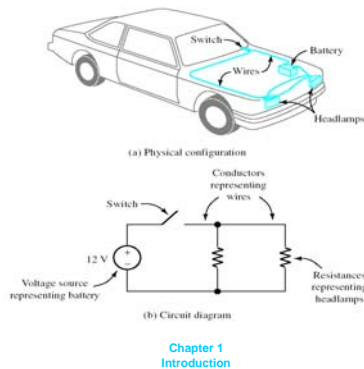

Electrical Circuit

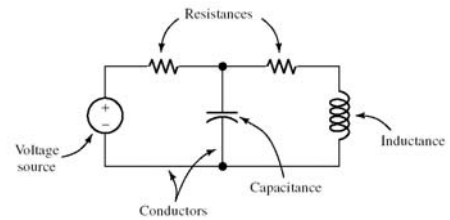

Basic Concepts

- Charge
- Current
- Voltage
- Power
- Energy

Chapter 1
Introduction

Basic Concepts: Charges

- Charge is an **electrical property** of the atomic particles which matter consists of, measured in coulombs (C)
- 1C of charge requires 6.24×10^{18} electrons
- **Law of conservation of charge**: charge **cannot** be **created** or **destroyed**, only transferred

Chapter 1
Introduction

Electric Current

- Electric current is the **rate of change** of charge, measured in amperes (A)

$$i(t) = \frac{dq(t)}{dt}$$

- 1 A = 1 C/s
- Two main types
 - **Direct current (DC)**: Current remains **constant**
 - **Alternating current (AC)**: Current varies **sinusoidally** with time

Chapter 1
Introduction

Examples: DC and AC Currents

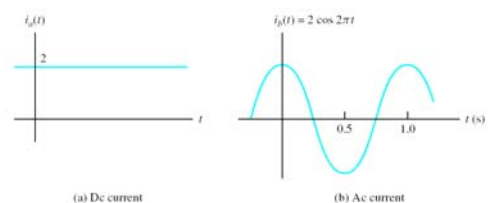


Figure 1.7 Examples of dc and ac currents versus time.

Chapter 1
Introduction

Notes on Current

- Current is physically realized by movement of **electrons**
- By convention, current direction is defined as flow of **positive** charges
- Positive charge is not flowing physically
- Electrons have a **negative** charge and move in the opposite direction of current

Chapter 1
Introduction

Safety Considerations

- Even small levels of current through the human body can cause serious, dangerous side effects
- Any current over **10 mA** is considered dangerous
- Currents of **50 mA** can cause severe shock
- Currents over **100 mA** can be fatal
- Treat electricity with respect – not fear

Chapter 1
Introduction

Other Forms of AC Current

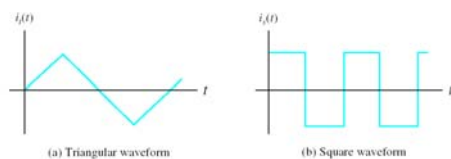


Figure 1.8 Ac currents can have various waveforms.

Chapter 1
Introduction

Reference Directions

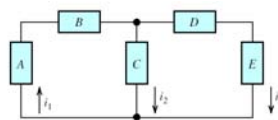


Figure 1.6 In analyzing circuits, we frequently start by assigning current variables i_1 , i_2 , i_3 , and so forth.

Chapter 1
Introduction

Voltage

- Voltage is the **energy** transferred as a unit of charge flows through a circuit element, measured in volts (V), which are equivalent to joules per coulomb (J/C)

$$v = \frac{dw}{dq}$$

- Analogous to **pressure** in a hydraulic system
- A measure of the **potential** between two points
- Voltage pushes charges in one direction

Chapter 1
Introduction

Reference Polarities

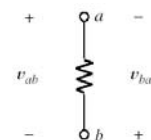


Figure 1.12 The voltage v_{ab} has a reference polarity that is positive at point a and negative at point b .

Chapter 1
Introduction

Power

- **Power**: **time rate** of expending or absorbing energy (watts)

$$p = \frac{dw}{dt}$$

- **By convention**:

Circuit elements that **absorb** power have a **positive** value

Circuit elements that **produce** power have a **negative** value

$$p(t) = \pm v(t)i(t)$$

Chapter 1
Introduction

Energy


- **Energy**: capacity to do work (joules)
- **Laws of conservation of energy**:
The **net** power absorbed by a circuit is equal to 0, or
The total energy produced in a circuit is equal to the total energy absorbed

$$w = \int_{t_1}^{t_2} p(t)dt \quad p = \frac{dw}{dt}$$

Chapter 1
Introduction

Passive Reference Configuration

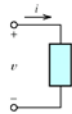
- **Passive sign convention**: Current enters the positive terminal of an element



$$p = vi$$

Chapter 1
Introduction

Example 1.2: Find power

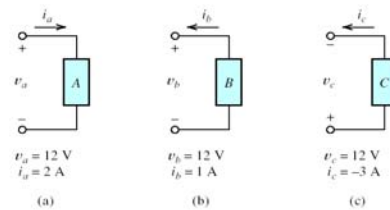

Chapter 1
Introduction

Circuit Laws

- **Kirchhoff's Current Law**
- **Kirchhoff's Voltage Law**
- **Ohm's Law**

Chapter 1
Introduction

Kirchhoff's current law

- A **node** is a point at which two or more circuit elements are joined together
- **Kirchhoff's Current Law (KCL)**: The **net** current entering a node is zero, or
- Alternatively, the sum of the currents entering a node equals the sum of the currents leaving a node

$$\sum_{m=1}^M I_m = 0$$

- Based on **law of conservation of charge**

Chapter 1
Introduction

Series circuits


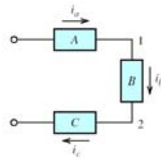


Figure 1.20 Elements A , B , and C are connected in series.


Chapter 1
Introduction

Exercise 1.7: Find currents

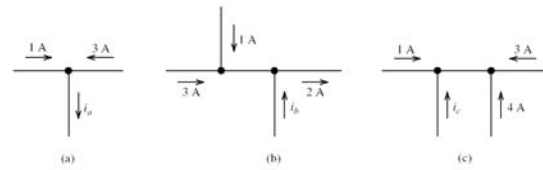

Chapter 1
Introduction

Exercise 1.8 – Identify elements in series

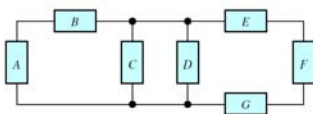

Chapter 1
Introduction

Kirchhoff's voltage law

- A **loop** is a closed path starting at a node and proceeding through circuit elements, eventually returning to the starting node
- Kirchhoff's voltage law (KVL)**: The **algebraic sum** of the voltages equals zero for any closed path (loop) in an electrical circuit


$$\sum_{m=1}^M V_m = 0$$

- Based on **law of conservation of energy**

Chapter 1
Introduction


Reference directions in applying KVL

Figure 1.24 In applying KVL to a loop, voltages are added or subtracted depending on their reference polarities relative to the direction of travel around the loop.

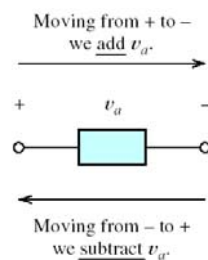

Chapter 1
Introduction

Example

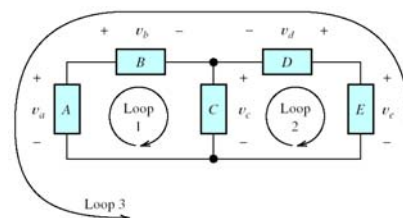

Chapter 1
Introduction

Parallel circuits


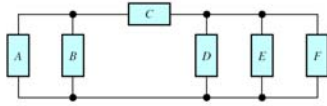


Figure 1.27 In this circuit, elements *A* and *B* are in parallel. Elements *D*, *E*, and *F* form another parallel combination.

Chapter 1
Introduction

Exercise 1.9 and 1.10

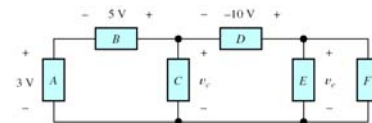

$$v_c = ? \quad v_e = ?$$

Chapter 1
Introduction

Independent voltage sources

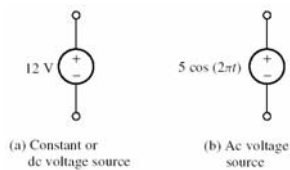


Figure 1.32 Independent voltage sources

Chapter 1
Introduction

Dependent voltage sources

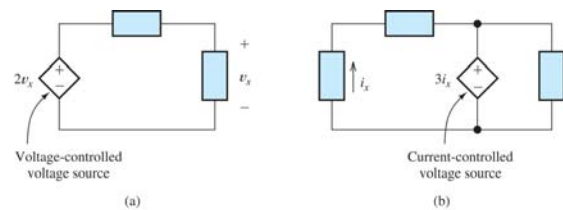


Figure 1.34 Dependent voltage sources (also known as controlled voltage sources) are represented by diamond-shaped symbols. The voltage across a controlled voltage source depends on a current or voltage that appears elsewhere in the circuit.

Chapter 1
Introduction

Independent current sources

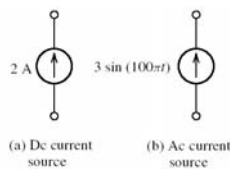


Figure 1.35 Independent current sources

Chapter 1
Introduction

Dependent current sources

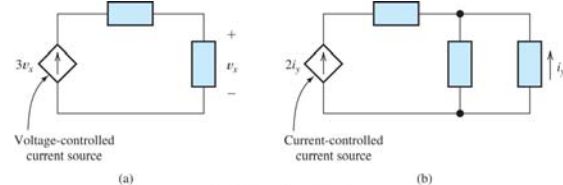


Figure 1.36 Dependent voltage sources. The current through a dependent current source depends on a current or voltage that appears elsewhere in the circuit.

Chapter 1
Introduction

Resistors and Ohm's Law




$$v = iR$$

$$v_{ab} = i_{ab}R$$

- Conductors (e.g. wires) have very low resistance that can be usually neglected
- Insulators (e.g. air) have very large resistance

Chapter 1
Introduction

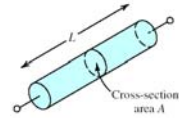Resistance Related to Physical Parameters



$$R = \frac{\rho L}{A}$$

Resistance of human body: ?

Chapter 1
Introduction

Other equations derived from Ohm's law

$$i = \frac{v}{R}$$

$$p = vi$$


$$R = \frac{v}{i}$$

$$p = \frac{v^2}{R}$$


$$p = i^2 R$$

Chapter 1
Introduction


Example: Simple circuit

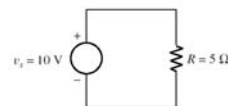


(a) Circuit diagram

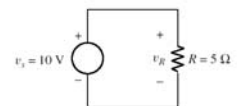

(b) KVL requires that $v_R = 10$ V

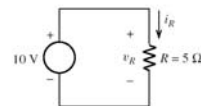

(c) Ohm's law yields $i_R = v_R/R = 2$ A

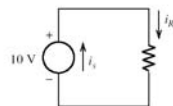

(d) KCL requires that $i_s = i_R$

Chapter 1
Introduction

Example: Find current and power


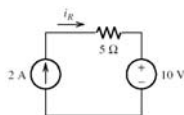


Fig.P1.62

Chapter 1
Introduction

Example: Find voltage

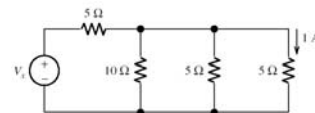

Animation for circuits:

<https://www.youtube.com/watch?v=m4jzgqZu-4s>

Chapter 1
Introduction