

Chapter 10 Amplifiers: Specifications and External Characteristics

1. Amplifier basic concepts.
2. Various amplifier models and analysis.
3. Importance of input and output impedances of amplifiers

Chapter 10
Amplifiers: Specifications and External Characteristics

Basic amplifier concepts

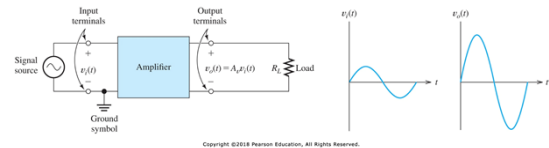


Figure 10.1 Electronic amplifier.

Chapter 10
Amplifiers: Specifications and External Characteristics

Basic amplifier concepts

Ideally, an amplifier produces an output signal with **identical** waveshape as the input signal, but with a **larger** amplitude.

$$v_o(t) = A_v v_i(t)$$

Chapter 10
Amplifiers: Specifications and External Characteristics

Typical examples

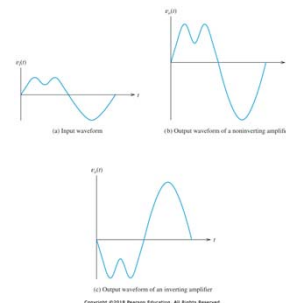


Figure 10.2 Input waveform and corresponding output waveforms.

Chapter 10
Amplifiers: Specifications and External Characteristics

Inverting versus Noninverting Amplifiers

Inverting amplifiers have **negative** voltage gain, and the output waveform is an inverted version of the input waveform.

Noninverting amplifiers have **positive** voltage gain.

Chapter 10
Amplifiers: Specifications and External Characteristics

Voltage-Amplifier Model

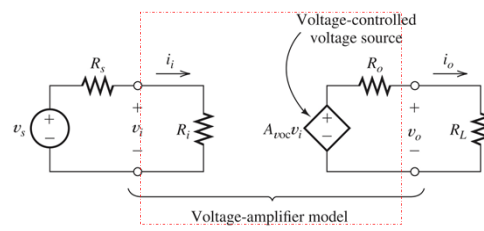


Figure 10.3 Model of an electronic amplifier, including input resistance R_i and output resistance R_o .

Chapter 10
Amplifiers: Specifications and External Characteristics

Current Gain

$$A_i = \frac{i_o}{i_i}$$

Chapter 10
Amplifiers: Specifications and External Characteristics

Power Gain

$$G = \frac{P_o}{P_i}$$

Chapter 10
Amplifiers: Specifications and External Characteristics

Example 10.1

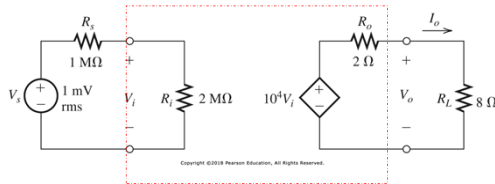


Figure 10.4 Source, amplifier, and load for Example 10.1.

Find A_i, G

Chapter 10
Amplifiers: Specifications and External Characteristics

$$V_i = \frac{R_i}{R_i + R_s} V_s = 0.667 \text{ mV}$$

$$V_o = A_{vo} V_i \frac{R_L}{R_L + R_o} = 5.33 \text{ V}$$

What is **loading** effect?

Chapter 10
Amplifiers: Specifications and External Characteristics

Cascaded amplifiers

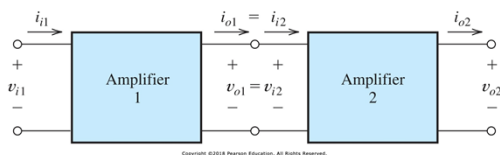


Figure 10.5 Cascade connection of two amplifiers.

$$A_v = A_{v1} A_{v2}$$

Chapter 10
Amplifiers: Specifications and External Characteristics

Example 10.2

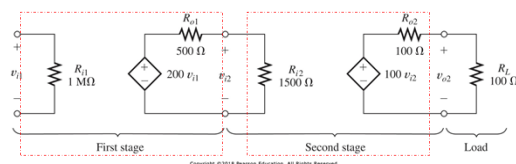


Figure 10.6 Cascaded amplifiers of Examples 10.2 and 10.3.

Find A_v, A_i, G

Chapter 10
Amplifiers: Specifications and External Characteristics

$$A_{v1} = \frac{v_{o1}}{v_{i1}} = \frac{v_{i2}}{v_{i1}} = A_{vo1} \frac{R_{i2}}{R_{i2} + R_{o1}} = 150$$

$$A_{v2} = \frac{v_{o2}}{v_{i2}} = A_{vo2} \frac{R_L}{R_L + R_{o2}} = 50$$

$$A_v = A_{v1} A_{v2} = 7500$$

$$A_{i1} = A_{v1} \frac{R_{i1}}{R_{i2}} = 10^5 \quad A_{i2} = A_{v2} \frac{R_{i2}}{R_L} = 750$$

$$A_i = A_{i1} A_{i2} = 75 \times 10^6$$

$$G_1 = A_{v1} A_{i1} = 1.5 \times 10^7 \quad G_2 = A_{v2} A_{i2} = 3.75 \times 10^4$$

$$G = G_1 G_2 = 5.625 \times 10^{11}$$

Chapter 10
Amplifiers: Specifications and External Characteristics

Simplified Models for Cascaded Amplifier

First, determine the voltage gain of the first stage accounting for **loading by the second stage**.

The **overall voltage gain** is the **product** of the gains of the separate stages.

The **input** impedance is that of the **first stage**, and the **output** impedance is that of the **last stage**.

Chapter 10
Amplifiers: Specifications and External Characteristics

Example 10.3

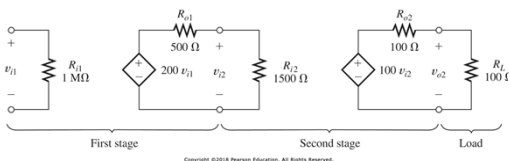


Figure 10.6 Cascaded amplifiers of Examples 10.2 and 10.3.

Chapter 10
Amplifiers: Specifications and External Characteristics

Example 10.3

$$A_{v1} = A_{vo1} \frac{R_{i2}}{R_{i2} + R_{o1}} = 150$$

$$A_{v2} = A_{vo2} = 100$$

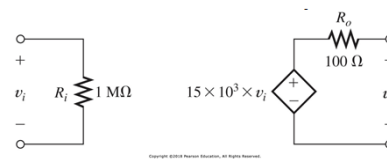


Figure 10.7 Simplified model for the cascaded amplifiers of Figure 10.6. See Example 10.3.

Chapter 10
Amplifiers: Specifications and External Characteristics

Current-Amplifier Model

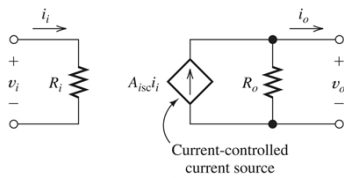


Figure 10.11 Current-amplifier model.

A_{isc} is the current gain of the amplifier with the output short circuited.

Chapter 10
Amplifiers: Specifications and External Characteristics

Example 10.5

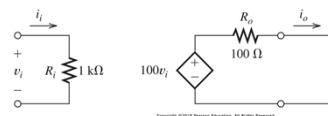


Figure 10.12 Voltage amplifier of Examples 10.5, 10.6, and 10.7.

$$i_i = \frac{v_i}{R_i}, \quad i_{osc} = \frac{A_{vo} v_i}{R_o}, \quad A_{isc} = \frac{i_{osc}}{i_i} = \frac{A_{vo} R_i}{R_o} = 10^3$$

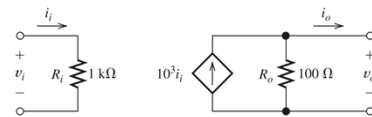


Figure 10.13 Current-amplifier model equivalent to the voltage-amplifier model of Figure 10.12. See Example 10.6.

Chapter 10
Amplifiers: Specifications and External Characteristics

Importance of amplifier impedances in various applications

Some applications call for amplifiers with **high** input impedance while others call for **low** input impedance.

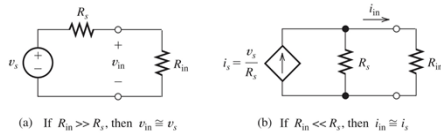


Figure 10.18 If we want to sense the open-circuit voltage of a source, the amplifier should have a high input resistance, as in (a). To sense the short-circuit current of the source, low input resistance is called for, as in (b).

Chapter 10
Amplifiers: Specifications and External Characteristics

Some applications call for amplifiers with **high** output impedance while others call for **low** output impedance.

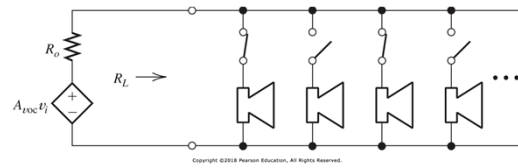


Figure 10.19 If the amplifier output resistance R_o is much less than the (lowest) load resistance, the load voltage is nearly independent of the number of switches closed.

Chapter 10
Amplifiers: Specifications and External Characteristics

Summary of Ideal amplifiers

Amplifier type	Input impedance	Output Impedance	Gain
Voltage	∞	0	A_{vo}
Current	0	∞	A_{isc}

Chapter 10
Amplifiers: Specifications and External Characteristics