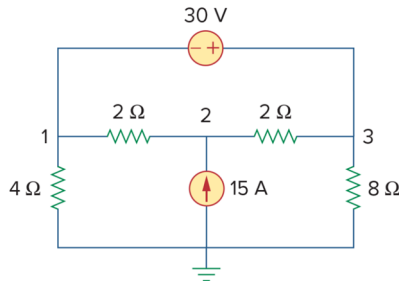



## EE1002 Principles of Electrical Engineering Assignment 2

(Questions from the Textbook by Alexander & Sadiku, 7<sup>th</sup> edition Problems 3.18, 3.43, 3.44, 4.39, 4.43, 4.51, 4.24, 4.40, and 4.48)


1. Determine the node voltages at nodes 1, 2, and 3 in the circuit in the following figure using nodal analysis.



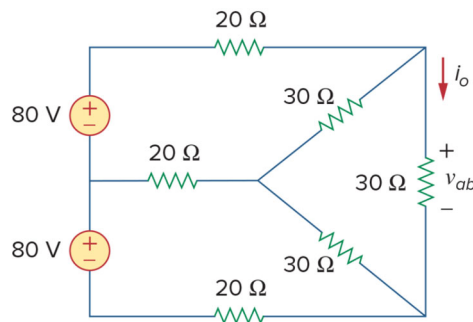
2. Use mesh analysis to find  $v_{ab}$  and  $i_o$  in the circuit in the following figure.



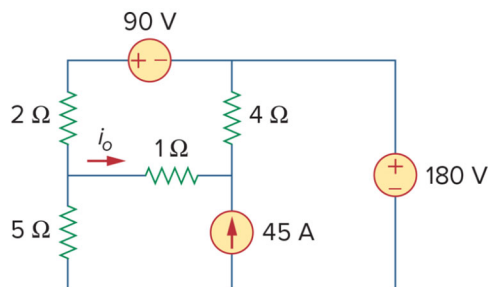
3. Use mesh analysis to obtain  $i_o$  in the circuit of the following figure.



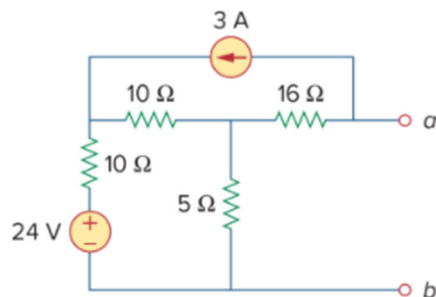
4. Obtain the Thevenin equivalent at terminals  $a-b$  of the following circuit.



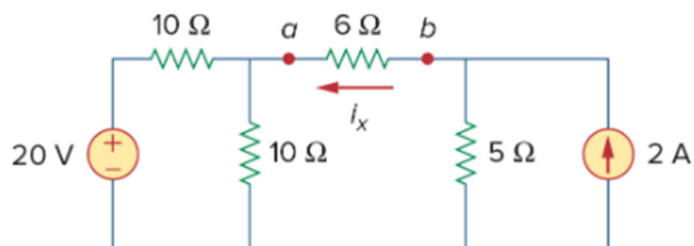
5. Find the Thevenin equivalent looking into terminals  $a$ - $b$  of the following circuit and solve for  $i_x$ .



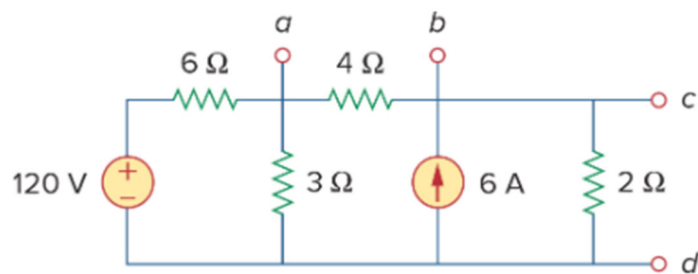6. Given the following circuit, obtain the Norton equivalent as viewed from terminals  
(a)  $a$ - $b$ ; and  
(b)  $c$ - $d$ .



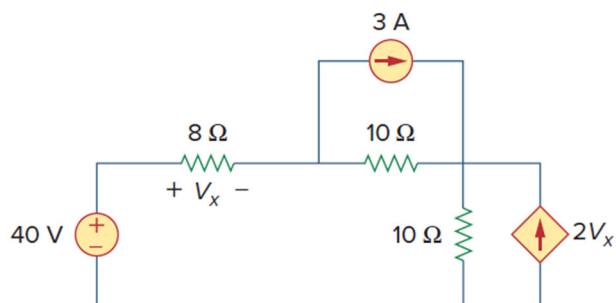7. Use source transformation to find the voltage  $V_x$  in the following circuit.



8. Find the Thevenin equivalent at terminals  $a$ - $b$  of the circuit in Fig. Q8.  
9. Determine the Norton equivalent at terminals  $a$ - $b$  for the circuit in Fig. Q9.

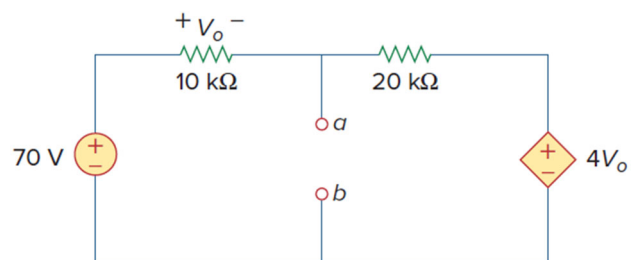


Fig. Q8

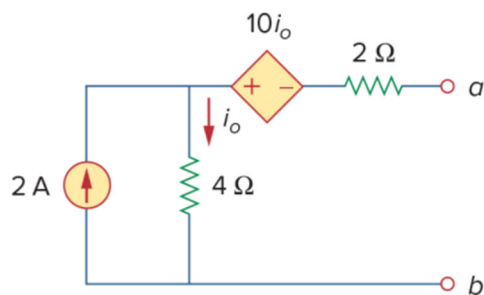


Fig. Q9